

## EE271 Lab Report 1

- a. Junchao Zhou EE271
- b. A 4:1 Mux is a device with four data inputs  $i00, i01, i10, i11$  and two selected input  $sel0$  and  $sel1$ . When  $sel0 == 0$  and  $sel1 == 0$ , the output is equal to the  $i00$  input. While  $sel0 == 1$  and  $sel1 == 0$ , the output is equal to the  $i01$  input. While  $sel0 == 0$  and  $sel1 == 1$ , the output is equal to the  $i10$  input. And while  $sel0 == 1$  and  $sel1 == 1$ , the output is equal to the  $i11$  input.
- c. True signal makes the LEDR's light up.
- d. The up position of the slider switch outputs a TRUE.
- e. The unpressed pushbutton outputs a TRUE.